



**Baker
College**

GREATNESS
IS EARNED HERE.

PLC Programming Instructions

Programmable Logic Controllers

Brad Peirson

College of Information Technology and Engineering

Agenda

PLC Data Types & Memory Architecture

Basic PLC Programming Instructions

PLC Timers and Counters

Advanced PLC Programming Instructions

Data Manipulation Instructions

Student Learning Outcomes

1. Create programs in Ladder Logic using the following instructions in an application
2. Program PLC timers and counters

PLC Data Types & Memory Architecture

PLC Data Types & Memory Architecture

Memory Hierarchy: Bits to Words

BIT

- 1 bit
- The smallest unit of memory
- Represents discrete binary states
 - 0 (OFF/FALSE)
 - 1 (ON/TRUE)

NIBBLE

- 4 bits
- 1 binary coded decimal (BCD) digit

BYTE

- 8 Bits
- 256 unique combinations
- Typically used for ASCII characters—1 BYTE = 1 character

WORD

- 16 Bits
- Historical standard register size in PLCs (AB SLC 500/Siemens S7-300)

DWORD/LWORD

- DWORD–32 bits
- LWORD–64 bits
- Modern architecture
- Used for high precision motion/math in older systems

Sub-Bit Access

- These data types are most often used as a number
- But they are *also* just a collection of bits
- We can access the individual bit inside a word using *dot notation*
 - `Word_Var.0`, `Word_Var.7`, etc.

IEC 61131-3 Elementary Types

Type	Keyword	Bits	Signed Range	Common Industrial Usage
Boolean	BOOL	1	0 or 1 (FALSE / TRUE)	Proximity sensors, pushbuttons, coils
Short Integer	SINT	8	-128 to +127	Small part counts, status flags
Integer	INT	16	-32,768 to +32,767	Analog inputs (0-10V, 4-20mA raw counts)
Double Integer	DINT	32	-2,147,483,648 to +2,147,483,647	High-speed encoders, totalizer counts
Real (Float)	REAL	32	IEEE 754 Floating Point	Scaled engineering units (PSI, GPM, °C)

Basic PLC Programming Instructions



The 3 Basic Instructions

- Ladder logic doesn't care what the input *is*
- All that matters is on/off
- Remember, these were intentionally designed to look like relay contacts and coils






Examine if Closed (XIC)

True when the input is true (on)

  



Examine if Open (XIO)

True when the input is false (off)

   





Output Energize (OTE)

True when the logic before it is true

  

Output Latch (OTL) and Unlatch (OTU)

    Once turned on the outputs *stays on* until explicitly unlatched



Take Caution with Latches

- Be *very* careful with latches—my recommendation is to not use them as much as possible
- OTE is *volatile*—when power cycles the output is set to 0 (off)
- OTL is *NOT* volatile—if it's on when power goes out it will be on when power is restored
- This can and has caused unwanted/unsafe machine motion



Latch/Unlatch on Key Platforms

How Key Platforms Handle Latch/Unlatch on Power Cycle

Manufacturer	Equivalent Instructions	Power Cycle Behavior	Memory Control Mechanism
Allen-Bradley (Logix5000)	OTL/OTU	Retains state across power cycles (non-volatile)	Tied directly to the instruction choice (OTL/OTU memory retention vs. OTE non-retention)
Siemens (TIA Portal)	S (Set)/ R (Reset)	Resets to 0 unless declared as Retentive	Bit/DB retain settings in tag table
Beckhoff (TwinCAT)/ CODESYS	S (Set)/ R (Reset)	Resets to 0 unless located in Retain memory	RETAIN or PERSISTENT keywords
Mitsubishi (GX Works)	SET/RST	Retains state if mapped to Latch Range	Latch (L) device memory range
Omron (Sysmac Studio)	Set/Rst	Resets to 0 unless declared as Retentive	Retain attribute checkbox on VAR

Oneshot

  A oneshot is true for *one scan* while the logic before it is true—the logic has to turn false to reset it



PLC Timers and Counters



Timers and Counters

- Timers time, counters count—but their under-the-hood structure is *very* similar
- “Timer” and “counter” refer to the *variable type*
- The timer or counter variable is then used in conjunction with a timer or counter instruction

Timer and Counter Variable Types

- Timers and counters are made up of 3 words:
 1. Word 0: Control word–used as bits, what the bits *do* vary between timers and counters
 2. Word 1: Preset (PRE)–the time/count target
 3. Word 2: Accumulated (ACC)–the current time/count

Timer Variables

- EN** Rung logic before the instruction is true
- TT** The timer is actively timing
- DN** The preset value has been reached
- PRE** The target time, in *milliseconds*
- ACC** The current timer value, in *milliseconds*

Timer Instructions


TON

Timer: My_Timer


PRE: 500

ACC: 0

TON Timing Diagram

 

TOF Timing Diagram

 

Counter Variables

CU The logic before the CTU instruction is true

CD The logic before the CTD instruction is true

DN The preset value has been reached


OV The ACC has exceeded the DINT limit of 2,147,483,647

UN The ACC has exceed the DINT limit of -2,147,483,648

PRE The target count


ACC The current count

CTU Timing Diagram

 

Advanced PLC Programming Instructions

Data Manipulation Instructions

 

Copyright Notice



PLC Programming Instructions©2026 by Brad Peirson is licensed under **CC BY-NC-SA 4.0**. To view a copy of this license, visit <https://creativecommons.org/licenses/by-nc-sa/4.0/>